

FD-PM1A

Technical Details & Schematic: AD8307 & LM3914 RF Power Meter

#### **REV1212**

## **Completed PM1A RF Power Meter and Field Strength Meter:**



#### **Project Details:**

In this project a quality Double Sided PTH Board is used measuring only 6.5cm x 11cm in size. Same good old AD8307 from Analog Devices is used (SO8 Package) for basic RF measurement up to 500MHZ. However instead of using a PIC and LCD, I am using a simple LM3914 Bar Graph IC for display of dbm levels.


Meter is powered from a 9V battery. A built-in 78L05 regulator is used to power AD8307.


10X LED is used with 4 green, 3 yellow and 3 Red LEDs indicating dbm from – 70dbm to +10dbm.

Header H1 is for changing the LED display from Dot to "Bargraph"...

Preset, CAL is available for calibration of measured this unit if you have an accurate measurement device handy!!
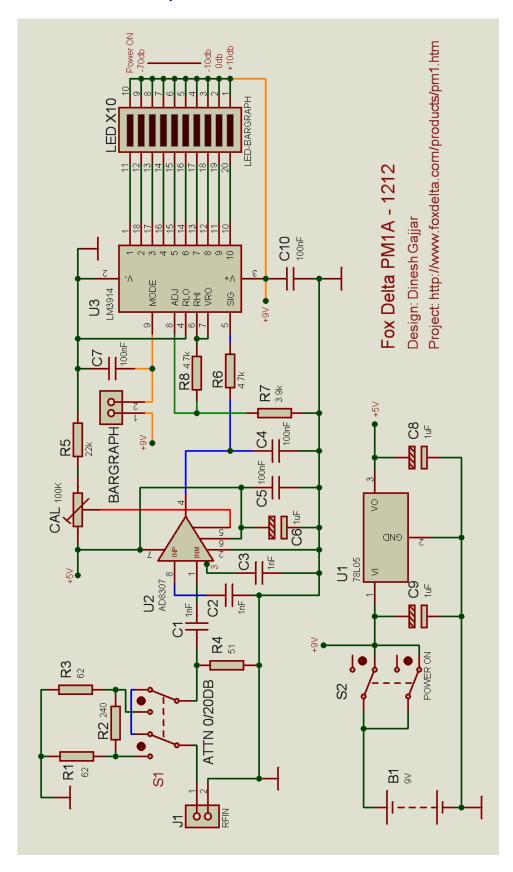
# Schematic of the simple AD8307 RF Meter: PM1A-1212



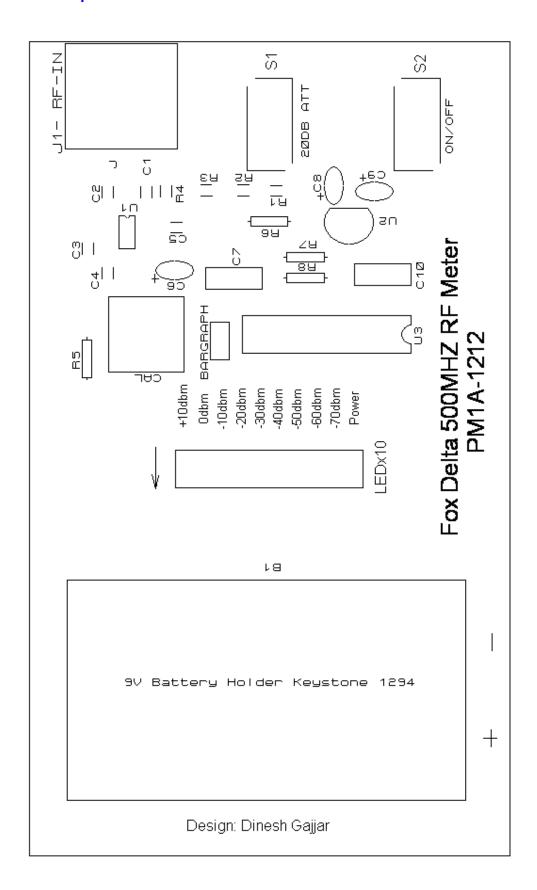

### **Kit Parts List:**

NIT Parts List:		
Quantity	Check	Part Name / Details
1		U3 IC LM3914 DIP18
1		U3 IC Socket 18pin
1		U1 AD8307 SO8
1		U2 78L05
1		J1 BNC R/A Socket
2		S1, 2 Push DPDT Switches
1		10XLED (SB1000SR1Y3G6 etc)
1		100K Preset (CAL)
1		PCB DSPTH PM1A-1212
2		0.1uf (C7, C10) Poly
3		1uf Tantalum (C6, 8, 9)
1		Battery Holder 9V
1		Free Metal Case (LED window need to be cut by user)
1		2PIN Header and shorting pin ("Bargraph")
1		Mounting Hardware for PCB
		Resistors 1/4W 5%
2		4.7K (R8, R6)
1		3.9K (R7)
1		2.2K (R5)
		SMT Parts – ALL 1206
2		62 ohms (R1, 3)
1		240 ohms (R2)
1		51 ohms (R4)
3		0.1uF (C3, 4, 5)
2		0.001uF (C1, 2)

S1 = 20db Attenuator S2 = Power ON/OFF



PM1A in a metal case. LEDs fitted on back of the board.

With in built battery, PM1A is a handy RF Field Strength Meter

73s Dinesh Gajjar 21<sup>st</sup> Dec 2012